



Course Name: Embedded Systems Design

Course Number: 14 : 332 : 493 : 03

Assignment: Lab 3 - Where No Clock Has Gone Before

Instructor: Southard

Date Submitted: 3/28/19

Submitted By: Fareen Pourmoussavian 165-00-7750

Electrical and Computer Engineering Department


School of Engineering

Rutgers University, Piscataway, NJ 08854

## Contents

Prelab .....	1
1 Purpose .....	2
2 Lab Assignment 1: We Can Rebuild Him .....	3
2.1 Theory of Operation .....	2
2.2 Design .....	3
2.3 Test .....	4
2.4 Implementation .....	7
3 Lab Assignment 2: We have the technology .....	10
3.1 Theory of Operation .....	10
3.2 Design .....	11
3.3 Implementation .....	16

## Prelab

 

# 1 Purpose

In this lab, we are introduced to the concept of a Finite State Machine (FSM) and we will use the FSM to create a common sequential design, a Universal Asynchronous Receiver Transmitter (UART). By using an FSM to control the behavior of a circuit in a certain sequence, we will be able to produce output that can be read by a computer and displayed in a terminal emulator.

## 2 Lab Assignment 1: We Can Rebuild Him

### 2.1 Theory of Operation

For data transmission, instead of sending multiple bits at once, one bit is sent at a time. This allows us to avoid using thousands of high frequency operating wires which suffer from a large amount of cross-talk and enables us to operate at higher transmission speeds. We do this by utilizing a UART and only have one wire for transmitting and one wire for receiving. To ensure things are sent and received in a consistent manner, the clock frequency must be the same for both wires. Therefore, it is asynchronous because both ends are operating on different clock domains.

For the UART, While the line is held high, no data is being transferred and the line is in an idle state. Once the line is low, that signifies the start of the data transmission. For the next data bits, clock cycles, we sample the line and store the char into a shift register (LSB is transmitted first). After data bits cycles, an optional parity bit is sent (usually XOR of the data bits). Finally, stop bits of logic high are sent to signify the end of the transmission.

## 2.2 Design

### UART\_tx

```
1  Library IEEE;
2  use ieee.std_logic_1164.all,ieee.numeric_std.all;
3
4  entity uart_tx is
5  port(clk,en,send,rst :in std_logic;
6       char :in std_logic_vector(7 downto 0);
7       ready,tx :out std_logic);
8  end uart_tx;
9
10 architecture uart_test of uart_tx is
11 type state_type is (IDLE,START,D);
12 signal P : state_type :=IDLE;
13 signal creg : std_logic_vector(7 downto 0);
14 signal count : std_logic_vector(2 downto 0);
15 begin
16   sync: process(clk)
17   begin
18     if(rising_edge(clk)) then
19       if(rst='1') then
20         P<=IDLE;
21         tx<='1';
22         creg<="00000000";
23         count<="000";
24         ready<='1';
25       elsif(en='1') then
26         case P is
27           When IDLE =>
28             if(send='1') then
29               tx<='0';
30               ready<='0';
31               creg<=char;
32               P<=start;
33             else
34               ready<='1';
35               tx<='1';
36             end if;
37           when START =>
38             count<="000";
39             tx<=creg(0);
40             creg<='0' & creg(7 downto 1);
41             P<=D;
42           when D=>
43             if (unsigned(count)<7) then
44               tx<=creg(0);
45               count<=std_logic_vector(unsigned(count)+1);
46               P<=D;
47               creg<='0' & creg(7 downto 1);
48             else
49               tx<='1';
50               P<=IDLE;
51             end if;
52           when others=>
53             P<=IDLE;
54         end case;
55       end if;
56     end if;
57   end process sync;
58 end architecture;
```

## 2.3 Test

### 2.3.1 Test Bench Code, UART

```
7  library IEEE;
8  use IEEE.std_logic_1164.all;
9  use ieee.numeric_std.all;
10
11  entity uart_tb is
12  end uart_tb;
13
14  architecture tb of uart_tb is
15
16      component uart port (
17          clk, en, send, rx, rst : in std_logic;
18          charSend               : in std_logic_vector(7 downto 0);
19          ready, tx, newChar     : out std_logic;
20          charRec                : out std_logic_vector(7 downto 0)
21      );
22  end component;
23
24  type str is array (0 to 4) of std_logic_vector(7 downto 0);
25  signal word : str := (x"48", x"65", x"6C", x"6C", x"6F");
26
27  signal rst : std_logic := '0';
28  signal clk, en, send, rx, ready, tx, newChar : std_logic := '0';
29  signal charSend, charRec : std_logic_vector(7 downto 0) := (others => '0');
30
31  begin
32
33      -- the sender UART
34      dut: uart port map(
35          clk => clk,
36          en => en,
37          send => send,
38          rx => tx,
39          rst => rst,
40          charSend => charSend,
41          ready => ready,
42          tx => tx,
43          newChar => newChar,
44          charRec => charRec);
45
46
47      -- clock process @125 MHz
48      process begin
49          clk <= '0';
50          wait for 4 ns;
51          clk <= '1';
52          wait for 4 ns;
53      end process;
54
55      -- en process @ 125 MHz / 1085 = ~115200 Hz
56      process begin
57          en <= '0';
58          wait for 8680 ns;
59          en <= '1';
```

```


60         wait for 8 ns;
61     end process;
62
63     -- signal stimulation process
64     process begin
65
66         rst <= '1';
67         wait for 100 ns;
68         rst <= '0';
69         wait for 100 ns;
70
71         for index in 0 to 4 loop
72             wait until ready = '1' and en = '1';
73             charSend <= word(index);
74             send <= '1';
75             wait for 200 ns;
76             charSend <= (others => '0');
77             send <= '0';
78             wait until ready = '1' and en = '1' and newChar = '1';
79
80             if charRec /= word(index) then
81                 report "Send/Receive MISMATCH at time: " & time'image(now) &
82                     lf & "expected: " &
83                     integer'image(to_integer(unsigned(word(index)))) &
84                     lf & "received: " & integer'image(to_integer(unsigned(charRec)))
85                     severity ERROR;
86             end if;
87
88         end loop;
89
90         wait for 1000 ns;
91         report "End of testbench" severity FAILURE;
92
93     end process;
94
95 end tb;
96

```




## 2.3.2 Simulation Results, UART

Ran for 5ms(exits early)

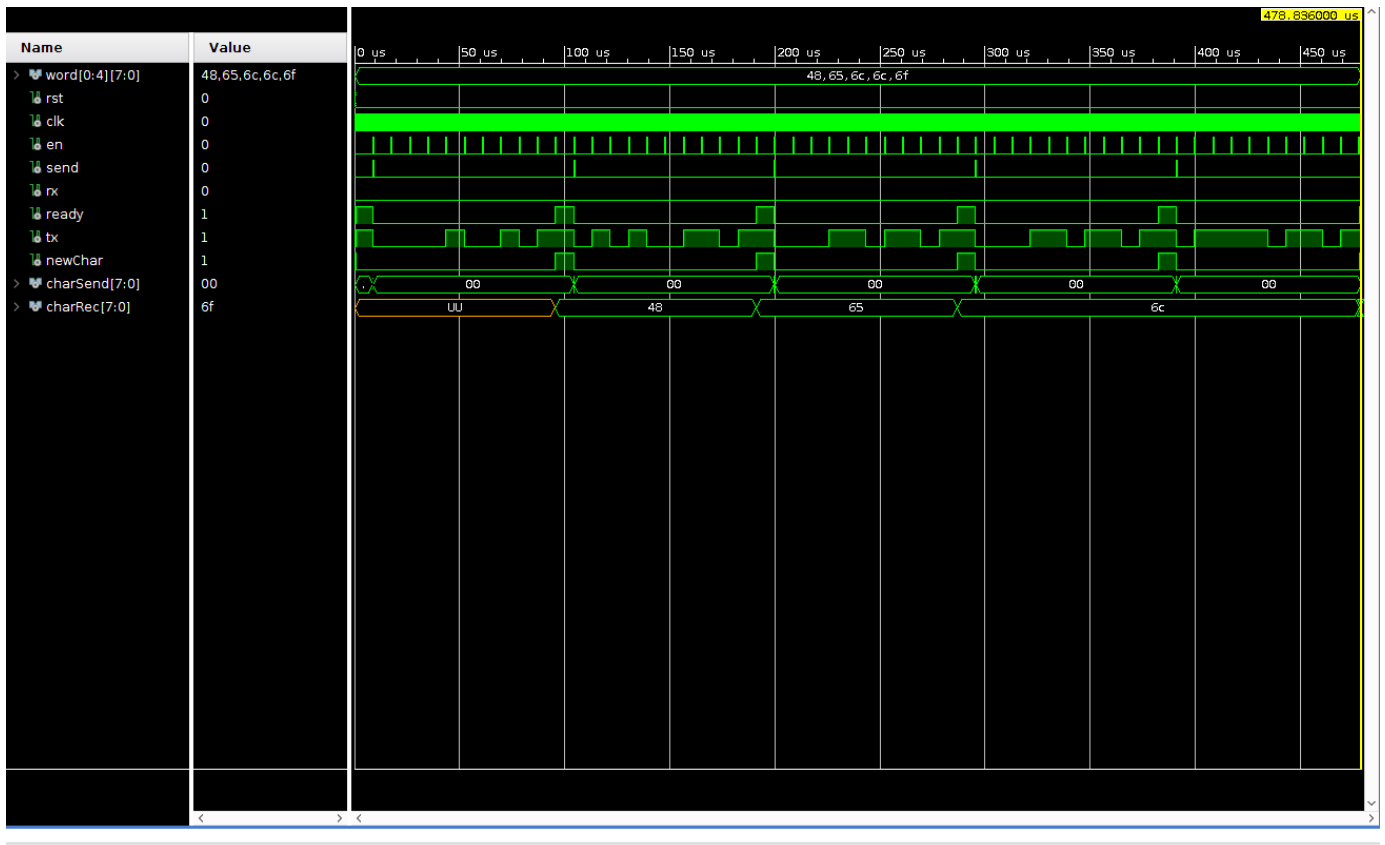


## 2.4 Implementation



### 2.4.1 Elaboration Schematic

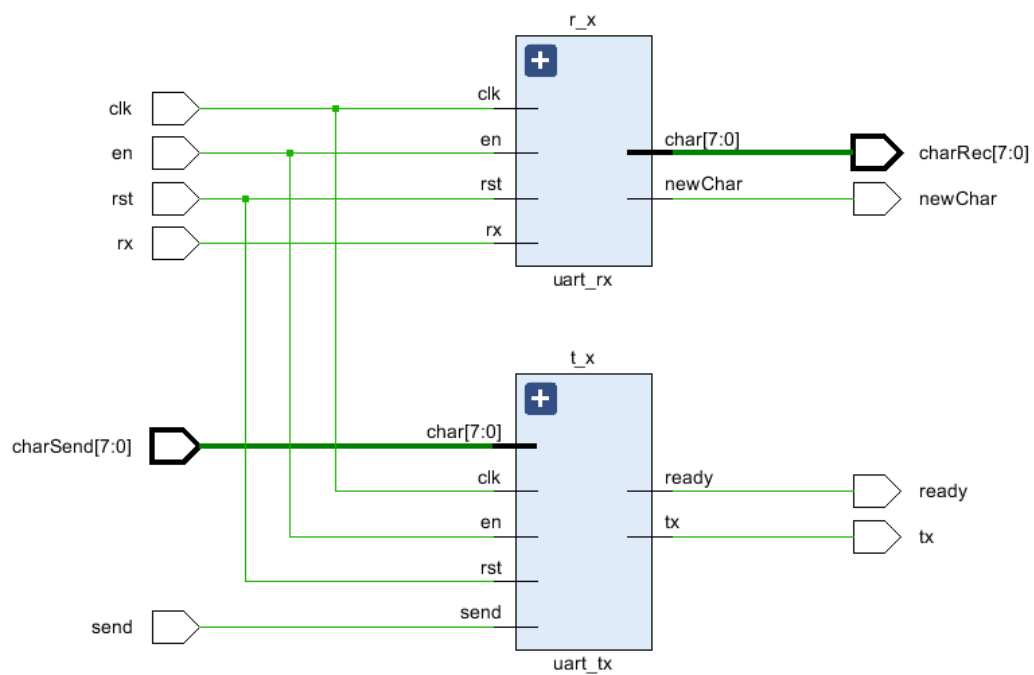

## 2.4.2 Synthesis Schematic

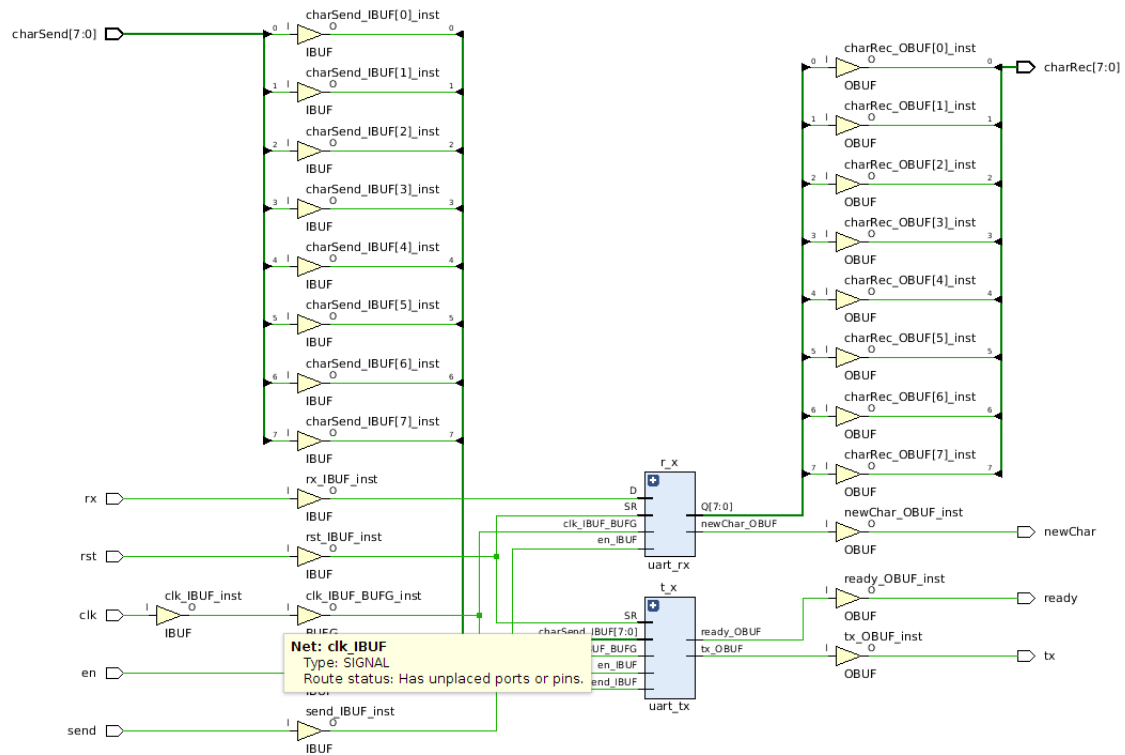

## 2.4.3 Project Summary

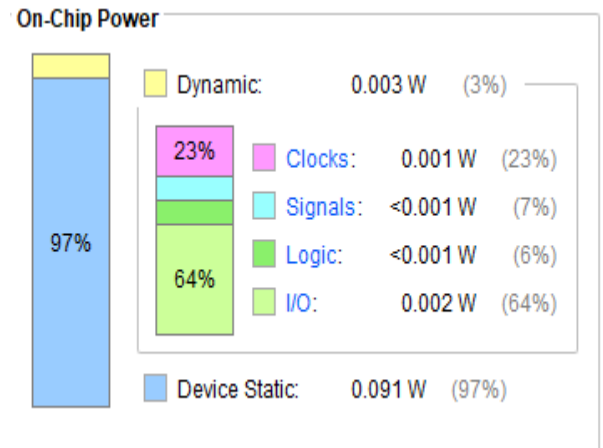 

## 2.4.4 Constraints

### 2.4.4 Constraints File

The 'clk' line of the document had to be uncommented. This was so that Vivado was able to extract pin information from the file. The rest of the lines were deleted, since they weren't needed.

```
1  ## This file is a general .xdc for the ZYBO Rev B board
2  ## To use it in a project:
3  ## - uncomment the lines corresponding to used pins
4  ## - rename the used signals according to the project
5
6
7  ##Clock signal
8  set_property -dict { PACKAGE_PIN L16   IOSTANDARD LVCMOS33 } [get_ports { clk }]; #IO_L11P_T1_SRCC_35 Sch=sysclk
9  create_clock -add -name sys_clk_pin -period 8.00 -waveform {0 4} [get_ports { clk }];
10
```

### 3 Lab Assignment 2: We have the technology

#### 3.1 Theory of Operation

In order to use the UART and talk to the computer, we need to drive some output through it by sending bytes. In order to do so, an FSM will be created which will drive the ASCII codes for my NetID along with a control signal to the UART. To have our UART work with the zybo board, we will need to use a USB UART pmod.

## 3.2 Design

### 3.2.1

#### Clk\_div

```
1  library ieee;
2  use ieee.std_logic_1164.all, ieee.numeric_std.all;
3
4  entity clk_div is
5  port(clk :in std_logic;
6        div :out std_logic);
7  end clk_div;
8
9  architecture clk of clk_div is
10 signal counter : std_logic_vector (25 downto 0) := (others => '0');
11 begin
12     process(clk)
13     begin
14         if(rising_edge(clk)) then
15             if(unsigned(counter)<1085) then
16                 counter <= std_logic_vector(unsigned(counter)+1);
17                 div <= '1';
18             else
19                 counter <= (others => '0');
20                 div <= '0';
21             end if;
22             if (unsigned(counter) = 543) then
23                 div <= '1';
24             else
25                 div <= '0';
26             end if;
27         end if;
28     end if;
29 end process;
30 end clk;
```

## Debouncer

```
1  library IEEE;
2  use ieee.std_logic_1164.all, ieee.numeric_std.all;
3
4  entity debounce is
5  port (clk : in std_logic;
6        btn : in std_logic;
7        dbnc : out std_logic);
8  end debounce;
9
10 architecture deb of debounce is
11 signal counter : std_logic_vector(22 downto 0);
12 signal btn_reg : std_logic_vector(1 downto 0);
13 begin
14
15     process (clk)
16     begin
17         if(rising_edge(clk)) then
18             btn_reg(0) <= btn; --bit 0 gets 1
19             btn_reg(1) <= btn_reg(0); --update bit 1 with bit 0 value
20             if(btn_reg(1)='1') then --if bit 1 is a 1 increment counter
21                 if(unsigned(counter)<25000000) then
22                     counter <= std_logic_vector(unsigned(counter)+1);
23                     dbnc <= '0';
24                 else
25                     dbnc <= '1';
26                 end if;
27             else --btn(1) == 0
28                 counter <= (others => '0');
29                 dbnc <= '0';
30             end if;
31         end if; --end if button pressed or not
32     end process;
33 end deb;
```

## Sender

```
1  library ieee;
2  use ieee.std_logic_1164.all, ieee.numeric_std.all;
3
4  entity sender is
5  port(btn,clk,en,rdy,rst : in std_logic;
6       char : out std_logic_vector(7 downto 0);
7       send : out std_logic);
8  end sender;
9
10 architecture send_test of sender is
11 type state_type is (IDLE,busyA,busyB,busyC);
12 signal N : state_type;
13 signal P : state_type :=IDLE; --initialized to IDLE
14 signal i : std_logic_vector(2 downto 0); --counts up to 5 cause FP183 is 5 characters
15 type id is array(0 to 4) of std_logic_vector(7 downto 0);
16 signal NETID : id := (X"66", X"70", X"31", X"38", X"33");
17 begin
18
19 sync: process(clk,en)
20 begin
21     if(rising_edge(clk) and en='1') then
22         if(rst='1') then
23             P<=IDLE;
24             i<="000";
25             char<="00000000";
26             send<='0';
27         end if;
28         case P is
29             when IDLE=>
30                 if(rdy='1' and btn='1' and unsigned(i)<5) then
31                     send<='1';
32                     char<=NETID(to_integer(unsigned(i)));
33                     i<=std_logic_vector(unsigned(i)+1);
34                     P<=busyA;
35                 elsif(rdy='1' and btn='1' and unsigned(i)=5) then
36                     i<="000";
37                     P<=IDLE;
38                 end if;
39             when busyA=>
40                 P<=busyB;
41             when busyB=>
42                 send<='0';
43                 P<=busyC;
44             when busyC=>
45                 if(rdy='1' and btn='0') then
46                     P<=IDLE;
47                 end if;
48             end case;
49         end if;
50     end process sync;
51 end send_test;
52
```

## Top\_level



```

1  library ieee;
2  use ieee.std_logic_1164.all, ieee.numeric_std.all;
3
4  entity top_lev is
5  port(TXD,clk: in std_logic;
6       btn : in std_logic_vector(1 downto 0);
7       RXD,RTS,CTS : out std_logic);
8  end top_lev;
9
10 architecture top_lev_crt of top_lev is
11 component clk_div
12     port(clk :in std_logic;
13          div :out std_logic);
14 end component;
15
16 component debounce
17     port(clk : in std_logic;
18          btn : in std_logic;
19          dbnc : out std_logic);
20 end component;
21
22 component sender
23     port(btn,clk,en,rdy,rst : in std_logic;
24          char : out std_logic_vector(7 downto 0);
25          send : out std_logic);
26 end component;
27
28 component UART
29 port(
30     clk, en, send, rx, rst      : in std_logic;
31     charSend                    : in std_logic_vector (7 downto 0);
32     ready, tx, newChar          : out std_logic;
33     charRec                     : out std_logic_vector (7 downto 0));
34 end component;
35
36 signal dbout1,dbout2,clk_out,red_out,send_out : std_logic;
37 signal char_out : std_logic_vector(7 downto 0);
38
39 begin
40
41 dbnc1 : debounce
42     port map(clk=>clk,
43             btn=>btn(0),
44             dbnc=>dbout1);
45
46 dbnc2 : debounce
47     port map(clk=>clk,
48             btn=>btn(1),
49             dbnc=>dbout2);
50 clk_divider : clk_div
51     port map(clk=>clk,
52             div=>clk_out);

```

```


52 |         div=>clk_out);
53 |
54 | send : sender
55 | port map(btn=>dbout2,
56 |         clk=>clk,
57 |         en=>clk_out,
58 |         rdy=>red_out,
59 |         rst=>dbout1,
60 |         char=>char_out,
61 |         send=>send_out);
62 | uart_blk : UART
63 | port map(charSend=>char_out,
64 |         clk=>clk,
65 |         en=>clk_out,
66 |         rst=>dbout1,
67 |         rx=>TXD,
68 |         send=>send_out,
69 |         ready=>red_out,
70 |         tx=>RXD);
71 | cts<='0';rts<='0'; --not sure what to set them to
72 | end top_lev_crt;
73 |

```


## 3.3 Implementation



### Elaboration Schematic

#### 3.3.1 Sender

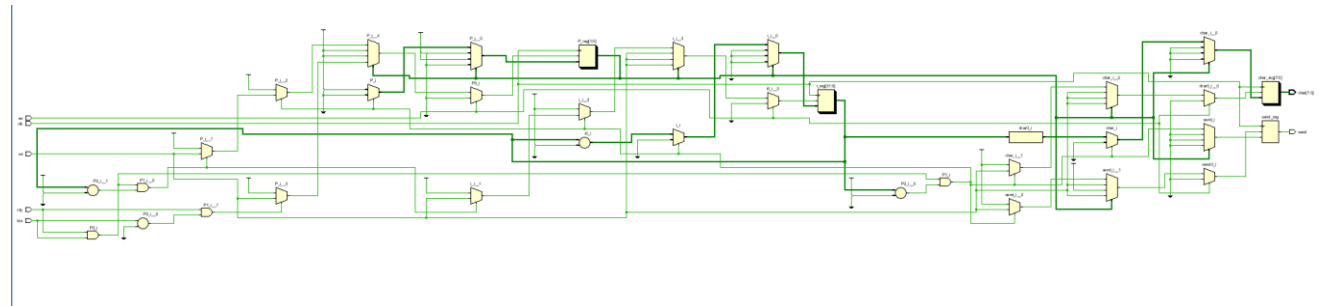

#### 3.3.1 Top Level

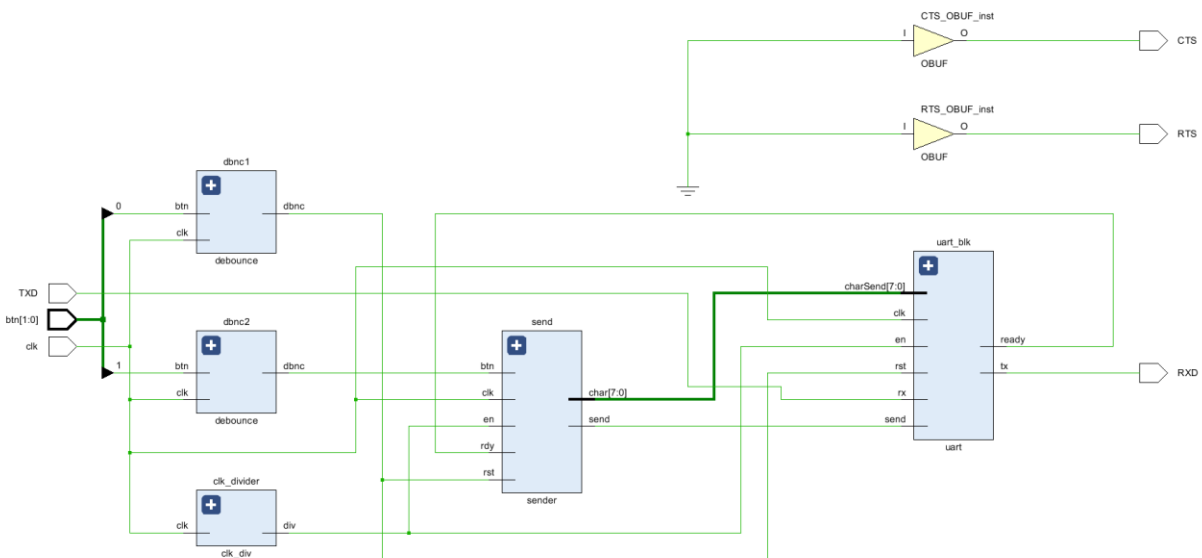


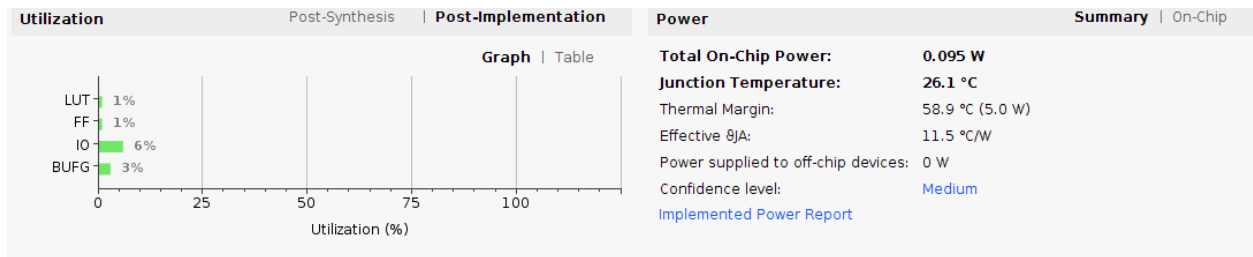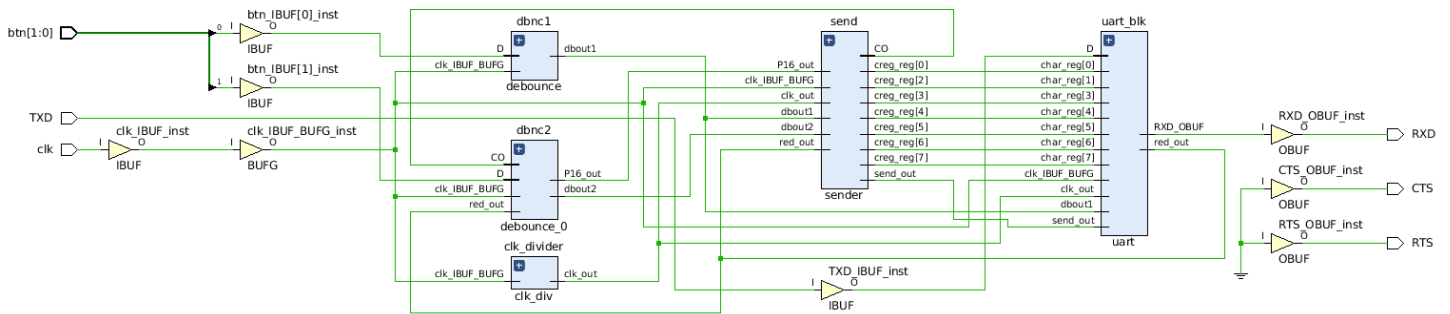

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

**Total On-Chip Power:** 0.095 W  
**Design Power Budget:** Not Specified  
**Power Budget Margin:** N/A  
**Junction Temperature:** 26.1°C  
Thermal Margin: 58.9°C (5.0 W)  
Effective  $\theta_{JA}$ : 11.5°C/W  
Power supplied to off-chip devices: 0 W  
Confidence level: Medium

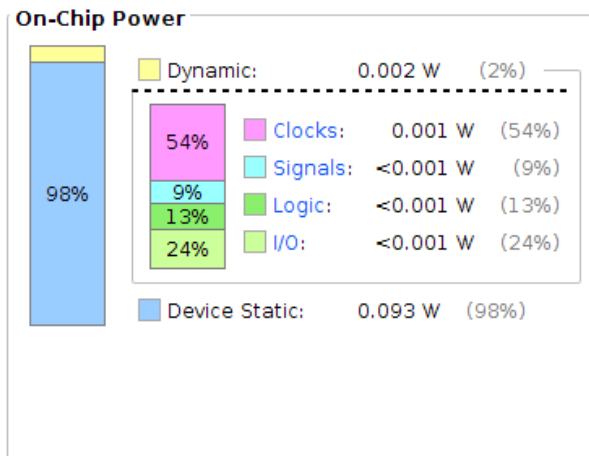[Launch Power Constraint Advisor](#) to find and fix invalid switching activity



### 3.3.4 Constraints File

I had to uncomment the clk, btn[1] and btn[0] as well as the first 4 JB pins and rename those parameters to the ones that correspond to the ones listed in the lab 3 manual